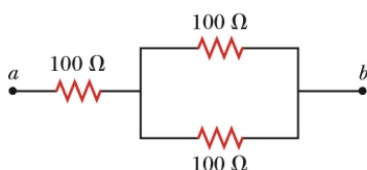


Problems


1. A battery has an emf of 15.0 V. The terminal voltage of the battery is 11.6 V when it is delivering 20.0 W of power to an external load resistor R . (a) What is the value of R ? (b) What is the internal resistance of the battery?

3. An automobile battery has an emf of 12.6 V and an internal resistance of 0.080 Ω . The headlights together have an equivalent resistance of 5.00 Ω (assumed constant). What is the potential difference across the headlight bulbs (a) when they are the only load on the battery and (b) when the starter motor is operated, with 35.0 A of current in the motor?


5. Three 100- Ω resistors are connected as shown in Figure P28.5. The maximum power that can safely be delivered to any one resistor is 25.0 W. (a) What is the maximum potential difference that can be applied to the terminals a and b ? (b) For the voltage determined in part (a), what is the power delivered to each resistor? (c) What is the total power delivered to the combination of resistors?



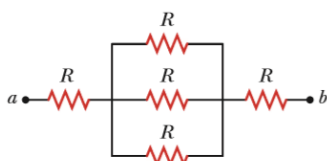
7. What is the equivalent resistance of the combination of identical resistors between points a and b in Figure P28.7?



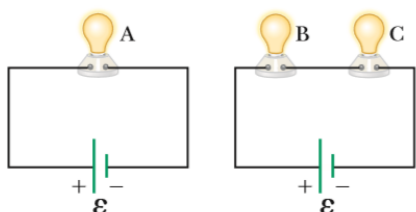8. Consider the two circuits shown in Figure P28.8 in which the batteries are identical. The resistance of each lightbulb is R . Neglect the internal resistances of the batteries. (a) Find expressions for the currents in each lightbulb. (b) How does the brightness of B compare with that of C? Explain. (c) How does the brightness of A compare with that of B and of C? Explain.




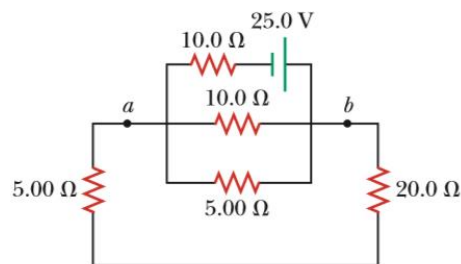9. Consider the circuit shown in Figure P28.9. Find (a) the current in the 20.0- Ω resistor and (b) the potential difference between points a and b .




10. (a) You need a 45- Ω resistor, but the stockroom has only 20- Ω and 50- Ω resistors. How can the desired resistance be achieved under these circumstances? (b) What can you do if you need a 35- Ω resistor?

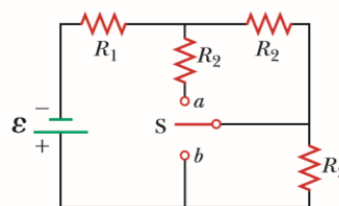11. A battery with $\mathcal{E} = 6.00$ V and no internal resistance supplies current to the circuit shown in Figure P28.11. When the double-throw switch S is open as shown in the figure, the current in the battery is 1.00 mA. When the switch is closed in position a , the current in the




battery is 1.20 mA. When the switch is closed in position b , the current in the battery is 2.00 mA. Find the resistances (a) R_1 , (b) R_2 , and (c) R_3 .

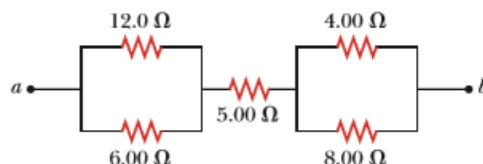17. Consider the combination of resistors shown in Figure P28.17. (a) Find the equivalent resistance between points a and b . (b) If a voltage of 35.0 V is applied between points a and b , find the current in each resistor.



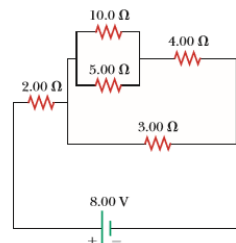21. Consider the circuit shown in Figure P28.21 on page 860. (a) Find the voltage across the 3.00- Ω resistor. (b) Find the current in the 3.00- Ω resistor.



- 1) 6.73, 1.97 Ω 3) 12.4, 9.6V 5) 75V, 6.25, 37.5 W 7) $7R/3$ 8) $A > B = C$ 9) 5.7V, 0.228 A
10) 45 Ω 35 Ω 11) 1k, 2k, 3k Ω 17) 11.67 Ω , $I_5 = 3A$ 21) 4.13 V, 1.38 A