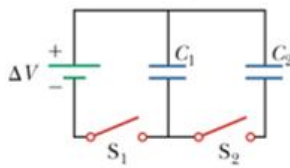


- 24.** Consider the circuit shown in Figure P26.24, where $C_1 = 6.00 \mu\text{F}$, $C_2 = 3.00 \mu\text{F}$, and $\Delta V = 20.0 \text{ V}$. Capacitor C_1

is first charged by closing switch S_1 . Switch S_1 is then opened, and the charged capacitor is connected to the uncharged capacitor by closing S_2 . Calculate (a) the initial charge acquired by C_1 and (b) the final charge on each capacitor.



- 37.** Two capacitors, $C_1 = 25.0 \mu\text{F}$ and $C_2 = 5.00 \mu\text{F}$, are connected in parallel and charged with a 100-V power supply. (a) Draw a circuit diagram and (b) calculate the total energy stored in the two capacitors. (c) **What If?** What potential difference would be required across the same two capacitors connected in series for the combination to store the same amount of energy as in part (b)? (d) Draw a circuit diagram of the circuit described in part (c).

- 43.** (a) How much charge can be placed on a capacitor with air between the plates before it breaks down if the area of each plate is 5.00 cm^2 ? (b) **What If?** Find the maximum charge if polystyrene is used between the plates instead of air.

- 48.** Each capacitor in the combination shown in Figure P26.48 has a breakdown voltage of 15.0 V. What is the breakdown voltage of the combination?

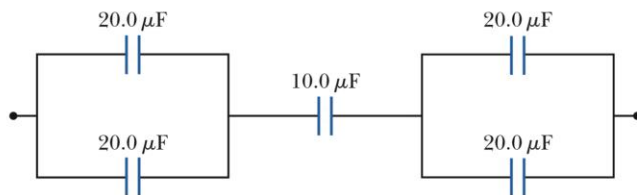


Figure P26.48

- 49.** A 2.00-nF parallel-plate capacitor is charged to an initial potential difference $\Delta V_i = 100 \text{ V}$ and is then isolated. The dielectric material between the plates is mica, with a dielectric constant of 5.00. (a) How much work is required to withdraw the mica sheet? (b) What is the potential difference across the capacitor after the mica is withdrawn?

- 67.** A capacitor of unknown capacitance has been charged to a potential difference of 100 V and then disconnected from the battery. When the charged capacitor is then connected in parallel to an uncharged $10.0\text{-}\mu\text{F}$ capacitor, the potential difference across the combination is 30.0 V. Calculate the unknown capacitance.

- 69.** Capacitors $C_1 = 6.00 \mu\text{F}$ and $C_2 = 2.00 \mu\text{F}$ are charged as a parallel combination across a 250-V battery. The capacitors are disconnected from the battery and from each other. They are then connected positive plate to negative plate and negative plate to positive plate. Calculate the resulting charge on each capacitor.

- 16.** A 0.900-V potential difference is maintained across a 1.50-m length of tungsten wire that has a cross-sectional area of 0.600 mm^2 . What is the current in the wire?

- 35.** At what temperature will aluminum have a resistivity that is three times the resistivity copper has at room temperature?

- 49.** A coil of Nichrome wire is 25.0 m long. The wire has a diameter of 0.400 mm and is at 20.0°C . If it carries a current of 0.500 A, what are (a) the magnitude of the electric field in the wire and (b) the power delivered to it? (c) **What If?** If the temperature is increased to 340°C and the potential difference across the wire remains constant, what is the power delivered?

- 66.** An all-electric car (not a hybrid) is designed to run from a bank of 12.0-V batteries with total energy storage of $2.00 \times 10^7 \text{ J}$. If the electric motor draws 8.00 kW as the car moves at a steady speed of 20.0 m/s, (a) what is the current delivered to the motor? (b) How far can the car travel before it is “out of juice”?

- 71.** An oceanographer is studying how the ion concentration in seawater depends on depth. She makes a measurement by lowering into the water a pair of concentric metallic cylinders (Fig. P27.71) at the end of a cable and taking data to determine the resistance between these electrodes as a function of depth. The water between the two cylinders forms a cylindrical shell of inner radius r_a , outer radius r_b , and length L much larger than r_b . The scientist applies a potential difference ΔV between the inner and outer surfaces, producing an outward radial current I . Let ρ represent the resistivity of the water. (a) Find the resistance of the water between the cylinders in terms of L , ρ , r_a , and r_b . (b) Express the resistivity of the water in terms of the measured quantities L , r_a , r_b , ΔV , and I .

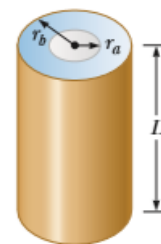


Figure P27.71

- 24) (120,40,80) μC 37) 0.150 J, 268 V 43) (13.3, 272) nC 48) 22.5 V 49) 40 μJ , 500 V 67) 4.29 μF
 69) (750, 250) μC 16) 6.43 A 35) 227 $^\circ\text{C}$ 49) 5.97 V/m, 75.5 W, 66 W 66) 667 A, 50.0 km